
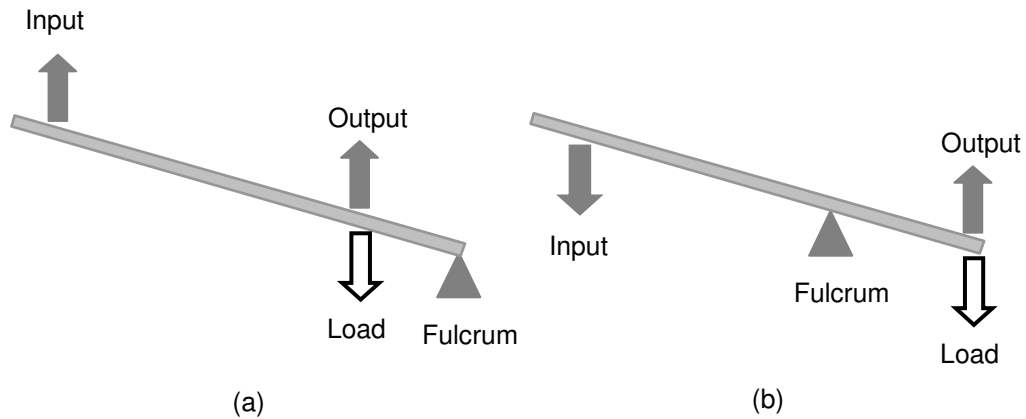


Answers to Exercises in Chapter 13

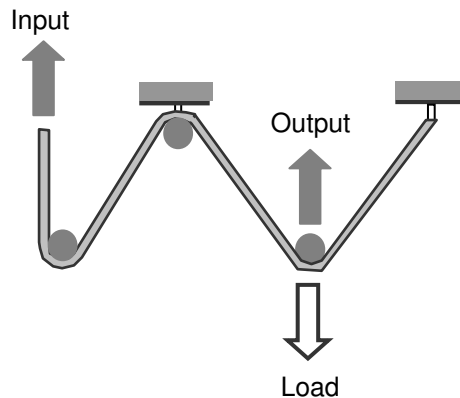- 13.1 Arrangement (a) below represents a non-inverting force amplifier and a non-inverting movement attenuator. (b) represents an inverting force amplifier and an inverting movement attenuator.



- 13.2 The arrangement below represents a non-inverting force amplifier.



- 13.3 Figure 13.2 is a non-inverting amplifier since the input and output are in the same direction. It could be transformed into an inverting amplifier simply by adding an extra half a turn of cable on the shaft. The input and output would then be in opposite directions.
- 13.4 The force applied to the brake pedal is being amplified to produce a larger force at the brake calliper (or other brake mechanism). This arrangement could also be seen as a displacement attenuator since the distance moved by the brake pedal (or the operator's foot) is much greater than that moved by the brake mechanism.

The source of power in power-assisted brakes is the engine.


13.5 Examples include:

Mechanical:	Passive:	Screw thread	Force	
	Active:	Slipping clutch	Force	Engine
Hydraulic:	Passive:	Hydraulic jack	Force	
	Active:	Hydraulic ram	Force	Pump
Pneumatic:	Passive:	Cycle pump	Pressure	
	Active:	Master/slave ram	Force	Pump
Electrical:	Passive:	Transformer (in text) – few others at this level		
	Active:	Photomultiplier	Current	PSU
Physiological:	Passive:	Lens of eye	Image size	
	Active:	Nerve synapse	Electrical energy	Chemical energy

13.6 25 V.

13.7 0.1.

13.8 Block diagram is as follows:

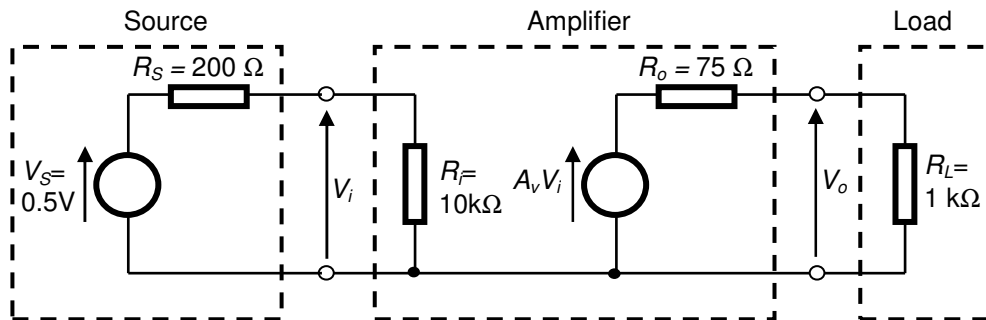

$$\begin{aligned}
 V_i &= \frac{R_i}{R_s + R_i} V_s \\
 &= \frac{10 \text{ k}\Omega}{200 \Omega + 10 \text{ k}\Omega} 0.5 \text{ V} \\
 &= 0.49 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 V_o &= A_v V_i \frac{R_L}{R_o + R_L} \\
 &= 20 V_i \frac{1 \text{ k}\Omega}{75 \Omega + 1 \text{ k}\Omega} \\
 &= 20 \times 0.49 \frac{1 \text{ k}\Omega}{75 \Omega + 1 \text{ k}\Omega} \\
 &= 9.12 \text{ V}
 \end{aligned}$$


13.9

$$\text{Voltage gain } (A_V) = \frac{V_o}{V_i} = \frac{9.12}{0.49} = 18.6$$

13.10 Input power $P_i = V_i^2/R_i = (0.49)^2/10^4 = 24 \mu\text{W}$. Output power $P_o = V_o^2/R_L = (9.12)^2/10^3 = 83 \text{ mW}$. Power gain = $P_o/P_i = 83 \text{ mW}/24 \mu\text{W} \approx 3.5 \times 10^3$.

13.11 The circuit of Exercises 13.8 and 13.9 can be produced by modifying the circuit of Computer Simulation Exercise 6.1.

13.12 Block diagram is as follows:

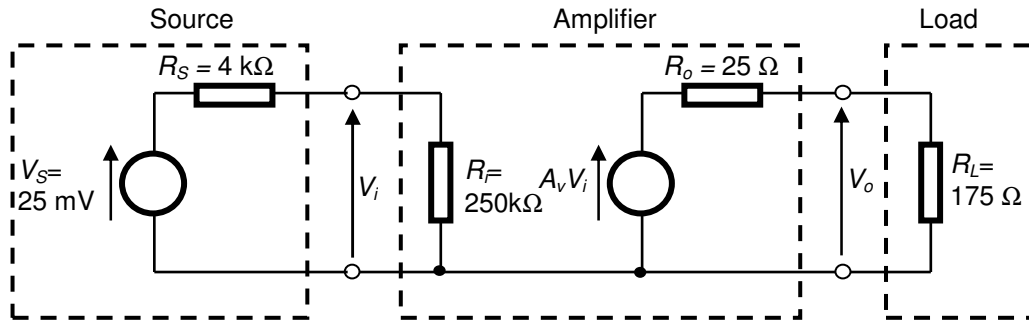

$$\begin{aligned} V_i &= \frac{R_i}{R_S + R_i} V_S \\ &= \frac{250 \text{ k}\Omega}{4 \text{ k}\Omega + 250 \text{ k}\Omega} 0.025 \text{ V} \\ &= 24.6 \text{ mV} \end{aligned}$$

$$\begin{aligned} V_o &= A_v V_i \frac{R_L}{R_o + R_L} \\ &= 500 V_i \frac{1 \text{ k}\Omega}{75 \Omega + 1 \text{ k}\Omega} \\ &= 500 \times 0.0246 \frac{175 \Omega}{25 \Omega + 175 \Omega} \\ &= 10.8 \text{ V} \end{aligned}$$


13.13

$$\text{Voltage gain } (A_V) = \frac{V_o}{V_i} = \frac{10.8}{0.0246} = 439$$

13.14 Input power $P_i = V_i^2/R_i = (0.0246)^2/(250 \times 10^3) = 2.4 \text{ nW}$.
Output power $P_o = V_o^2/R_L = (10.8)^2/175 = 667 \text{ mW}$.
Power gain = $P_o/P_i = 667 \text{ mW}/2.4 \text{ nW} \approx 2.8 \times 10^8$.

13.15 The circuit of Exercises 13.12 and 13.13 can be produced by modifying the circuit of Computer Simulation Exercise 13.1.

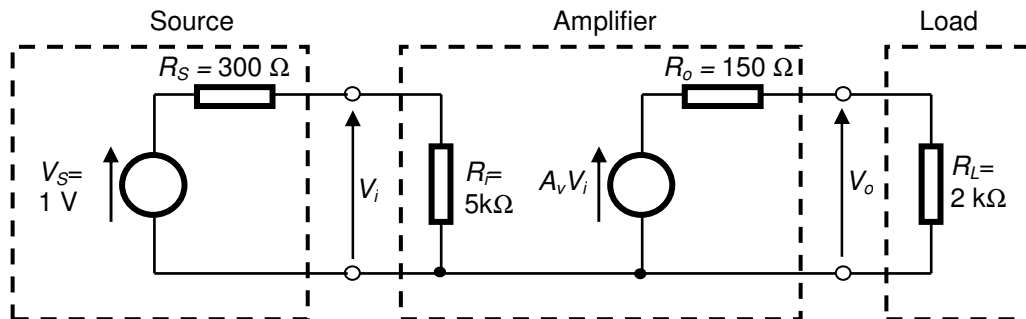- 13.16 The sensor produces an output voltage of 10 mV/cm. Therefore, for a displacement of 1 m the output will be 1 V. Therefore the block diagram is as follows:



$$\begin{aligned} V_i &= \frac{R_i}{R_S + R_i} V_S \\ &= \frac{5\text{ k}\Omega}{300\ \Omega + 5\text{ k}\Omega} 1\text{ V} \\ &= 943\text{ mV} \end{aligned}$$

$$\begin{aligned} V_o &= A_v V_i \frac{R_L}{R_o + R_L} \\ &= 15 V_i \frac{2\text{ k}\Omega}{150\ \Omega + 2\text{ k}\Omega} \\ &= 15 \times 0.943 \frac{2\text{ k}\Omega}{150\ \Omega + 2\text{ k}\Omega} \\ &= 13.2\text{ V} \end{aligned}$$

- 13.17 The circuit of Exercise 13.16 can be produced by modifying the circuit of Computer Simulation Exercise 13.1.
- 13.18 Overall gain = 25 + 15 – 10 = 30 dB.
- 13.19 The gain at the upper cut-off will be 3 dB lower than the mid-band gain. Therefore the gain at the cut-off is 22 dB.
- 13.20 A voltage gain of 10 is a gain of 20 dB. The gain at the upper cut-off will be 3 dB lower than the mid-band gain. Therefore the gain at the cut-off is 17 dB or 7.07.
- 13.21 The bandwidth is the difference between the upper and lower cut-off frequencies. Here it is 25 kHz – 1 kHz = 24 kHz.
- 13.22 Here the bandwidth is equal to the upper cut-off frequency, which is 5 MHz.

- 13.23 The input voltage of a differential amplifier is the difference between its two input voltages (V_+ - V_-). In this case it is $18.3 - 18.2 = 0.1$ V. Therefore the output voltage will be given by $V_o = A_v V_i = 100V_i = 10$ V.
- 13.24 The maximum voltage will be the supply voltage V and the minimum (that is, the most negative) voltage will be 0 V.