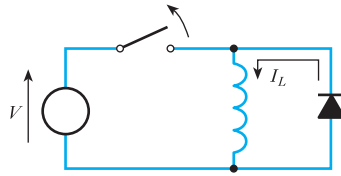


Figure 16.24 Use of a catch diode.



the diode, which then conducts and dissipates the stored energy. The diode must be able to handle a current equal to the forward current flowing before the supply is removed.

Key points


- Semiconductor materials are used at the heart of a multitude of electronic devices.
- The electrical properties of materials are brought about by their atomic structure.
- At very low temperatures semiconductors have the properties of an insulator. At higher temperatures thermal vibration of the atomic lattice leads to the generation of mobile charge carriers.
- Pure semiconductors are poor conductors, even at high temperatures. However, the introduction of small amounts of impurities dramatically changes their properties.
- Doping of semiconductors with appropriate materials can lead to the production of n -type or p -type materials.
- A junction between n -type and p -type semiconductors (a pn junction) has the properties of a diode.
- Semiconductor diodes approximate ideal diodes, but have a conduction voltage. Silicon diodes have a conduction voltage of about 0.7 V.
- In addition to conventional pn junction diodes, there are a wide variety of more specialised diodes, such as Zener, Schottky, tunnel and varactor diodes.
- Diodes are used in a range of applications, in both analogue and digital systems, including rectification, demodulation and signal clamping.

Exercises

- 16.1** Describe briefly the electrical properties of conductors, insulators and semiconductors.
- 16.2** Name three materials commonly used for semiconductor devices. Which material is most widely used for this purpose?
- 16.3** Outline the effect of an applied electric field on free electrons and holes.
- 16.4** Explain, with the aid of suitable diagrams where appropriate, what is meant by the terms ‘tetravalent material’, ‘covalent bonding’ and ‘doping’.
- 16.5** What are meant by the terms ‘intrinsic conduction’ and ‘extrinsic conduction’? What form of charge carriers is primarily responsible for conduction in doped semiconductors?




Exercises continued

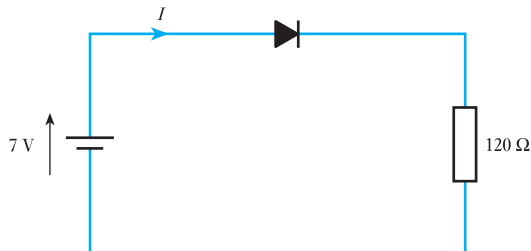- 16.6** Explain what is meant by a depletion layer and why this results in a potential barrier.
- 16.7** Explain the diode action of a pn junction in terms of the effects of an external voltage on the drift and diffusion currents.
- 16.8** Sketch the current–voltage characteristic of a silicon diode for both forward- and reverse-bias conditions.
- 16.9** Sketch the current–voltage characteristic of an ideal diode.
- 16.10** What is the difference between a diode and a rectifier?
- 16.11** What is meant by the reverse saturation current of a diode?
- 16.12** Explain what is meant by the turn-on voltage and the conduction voltage of a diode. What are typical values of these quantities for a silicon diode?
- 16.13** What are typical values for the turn-on voltage and conduction voltage of diodes formed from germanium and gallium arsenide?
- 16.14** Explain the use of equivalent circuits of diodes and give examples of diode equivalent circuits of different levels of sophistication.
- 16.15** Use computer simulation to plot the characteristic of a typical silicon diode, such as a 1N4002, and use this to determine appropriate values for V_{ON} and r_{ON} . Assume that the diode is to be used in a circuit where the quiescent current through the diode will be approximately 20 mA, then construct an equivalent circuit of the diode when used in such a circuit.
- 16.16** Repeat the previous exercise using a different diode, such as a 1N914, and compare your results.
- 16.17** Explain, with the aid of a suitable sketch, how you would use load line analysis to determine the current I in the following circuit.





- 16.18** Estimate the current in the circuit of the previous exercise, assuming that the diode can be adequately represented by an equivalent circuit consisting of an ideal diode and a fixed voltage source.

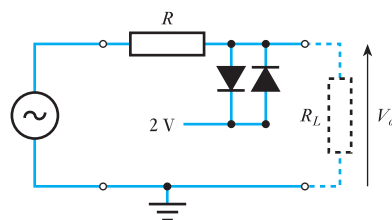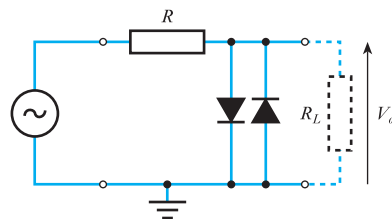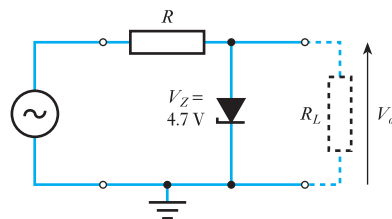- 16.19** Explain the terms ‘Zener breakdown’ and ‘avalanche breakdown’.
- 16.20** Sketch a simple circuit that uses a Zener diode to produce a constant output voltage of 5.6 V from an input voltage that may vary from 10 to 12 V. Select appropriate component values, such that the circuit will deliver a current of at least 100 mA to an external load, and estimate the maximum power dissipation in the diode.
- 16.21** A half-wave rectifier is connected to a 50 Hz supply and generates a peak output voltage of 100 V across a 220 μF reservoir capacitor. Estimate the peak ripple voltage produced if this arrangement is connected to a load that takes a constant current of 100 mA.
- 16.22** What would be the effect on the ripple voltage calculated in the last exercise of replacing the half-wave rectifier with a full-wave rectifier of similar peak output voltage?
- 16.23** Sketch the output waveforms of the following circuits. In each case, the input signal is a sine wave of ± 5 V peak.



Exercises continued

- 16.24**  Use circuit simulation to verify your answers to the last exercise. How does the value of R_L affect the operation of the circuits?
- 16.25** Design a circuit that will pass a signal unaffected, except that it limits its excursion to the range $+10.4 \text{ V} > V > -0.4 \text{ V}$.
- 16.26**  Use circuit simulation to verify your solution to the last exercise.