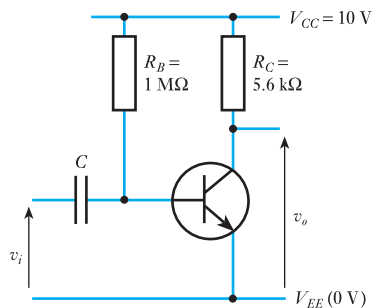


blocking any DC component that would upset the biasing. Unfortunately, the use of capacitors restricts the low-frequency performance of the arrangement and produces a complicated and bulky circuit.

- An alternative method is to use direct coupling between stages. This requires fewer components and permits operation down to DC.
- Bipolar transistors are used in a wide range of applications in addition to their use as simple amplifiers. More complicated circuits, such as operational amplifiers and other integrated circuits, are often constructed using bipolar transistors.


Exercises

- 18.1** Why are bipolar transistors so called?
- 18.2** Is a bipolar transistor a voltage-controlled or a current-controlled device?
- 18.3** Sketch the relationship between the base current and the collector current in a bipolar transistor (when the device is in its normal operating environment).
- 18.4** Sketch the construction of the two polarities of bipolar transistor.
- 18.5** What is meant by the symbols V_{CC} , V_{CE} , V_{BE} , v_{be} and i_c ?
- 18.6** Explain what is meant by ‘transistor action’.
- 18.7** Explain the terms h_{FE} and h_{fe} and describe their relative magnitudes.
- 18.8** Sketch the relationship between the base voltage and the collector current in a bipolar transistor (when the device is in its normal operating environment).
- 18.9** What is meant by the transconductance of a transistor? How does this quantity relate to the characteristic described in the previous exercise?
- 18.10** Determine the quiescent collector current and the quiescent output voltage of the following circuit, given that the h_{FE} of the transistor is 100.




- 18.11** Repeat Exercise 18.10, but replace the transistor with one that has a current gain of 200. Is this circuit useful as an amplifier?

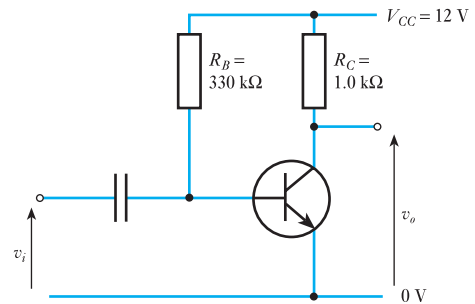- 18.12** Derive a simple small-signal equivalent circuit for the following circuit, then deduce the small-signal voltage gain, input resistance and output resistance, given that $h_{FE} \approx h_{fe} = 175$ and $h_{oe} = 15 \mu\text{S}$. How is the small-signal voltage gain related to the quiescent voltage across R_C ?




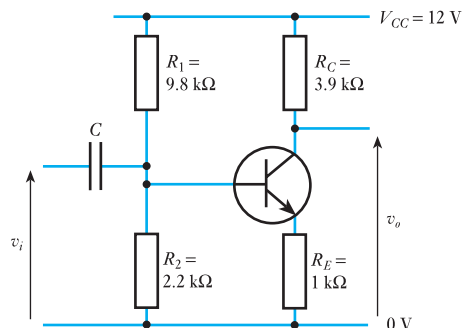- 18.13** Repeat the calculations of Exercise 18.12, this time assuming that the transistor has $h_{oe} = 330 \mu\text{S}$.
- 18.14** Calculate the quiescent collector current, quiescent output voltage and small-signal voltage gain of the following circuit.




Exercises continued

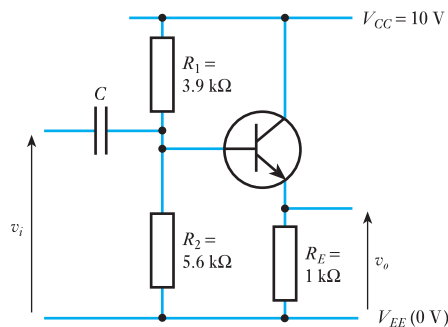- 18.15** For the circuit of Exercise 18.14, estimate the small-signal input and output resistance.
- 18.16** For the circuit of Exercise 18.14, estimate the effect on the frequency response of the circuit of using a coupling capacitor C of $1\ \mu\text{F}$.
- 18.17** Use simulation to confirm your answers to Exercises 18.14 and 18.16.
- 18.18** If the circuit of Exercise 18.14 were modified by the addition of an emitter decoupling capacitor of $10\ \mu\text{F}$, estimate the quiescent output voltage, small-signal voltage gain and low-frequency cut-off of the resulting circuit. What would be a suitable value for the decoupling capacitor if the amplifier were required for use with signals down to $100\ \text{Hz}$?
- 18.19** Use simulation to confirm your answers to Exercise 18.18.
- 18.20** Using a circuit of the form shown in Exercise 18.14, design an amplifier with a small-signal voltage gain of -3 , quiescent output voltage of $7\ \text{V}$, supply voltage of $12\ \text{V}$ and collector load resistance of $2.2\ \text{k}\Omega$.
- 18.21** Use simulation to confirm the operation of your solution to Exercise 18.20.
- 18.22** For the amplifier designed in Exercise 18.20, calculate the small-signal input resistance and then determine an appropriate value for the input capacitor to allow satisfactory operation at frequencies down to $50\ \text{Hz}$.
- 18.23** Calculate the quiescent collector current, quiescent output voltage and small-signal voltage gain of the following circuit.



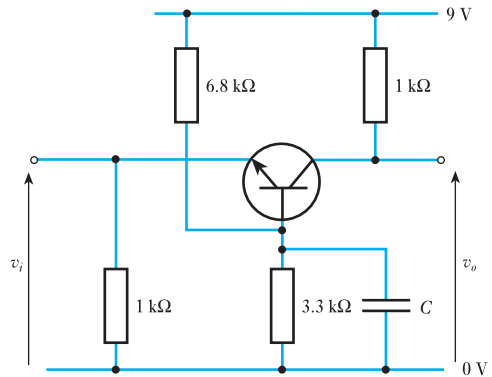- 18.24** Estimate the input resistance of the circuit in Exercise 18.23, then determine an appropriate value for a coupling capacitor to allow satisfactory operation down to $50\ \text{Hz}$.
- 18.25** Use simulation to confirm your answers to Exercises 18.23 and 18.24.
- 18.26** Determine the quiescent output voltage, voltage gain and input and output resistance of the following circuit. You may find it helpful to redraw the circuit in a more familiar form. You may assume that the capacitor C has a negligible impedance at the frequencies of interest.



- 18.27** Design a two-stage, direct-coupled amplifier with a voltage gain of 10. The circuit should operate from a $15\ \text{V}$ supply and have a maximum output swing of at least $4\ \text{volts}$ peak to peak.
- 18.28** Use simulation to investigate the performance of your solution to the previous exercise.
- 18.29** Design a long-tailed pair amplifier based on the circuit of Figure 18.38 and use simulation to determine the small-signal voltage gain of the circuit and its CMRR.