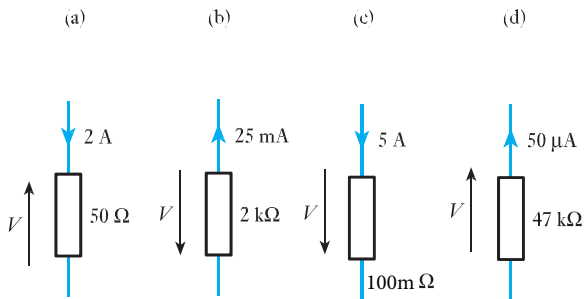



TUTORIAL 3 RESISTANCE AND DC CIRCUITS

- 3.1 Write down an equation relating current and charge.
- 3.2 What quantity of charge is transferred if a current of 5 A flows for 10 seconds?
- 3.3 What is the internal resistance of an ideal voltage source?
- 3.4 What is meant by a *controlled* voltage source?
- 3.5 What is the internal resistance of an ideal current source?
- 3.6 Determine the voltage V in each of the following circuits, being careful to note its polarity in each case.




- 3.7 For each circuit in exercise 3.6, determine the power dissipated in the resistor.
- 3.8 Estimate the resistance of a copper wire with a cross-sectional area of 1 mm^2 and a length of 1 m at 20°C .
(resistivity of copper at 20 degrees is $1.68 \times 10^{-8} \text{ ohm m}$)

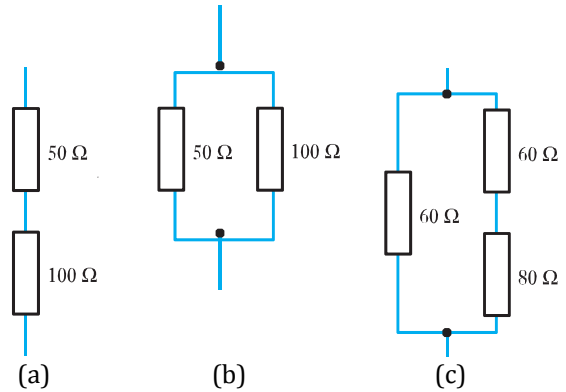
- 3.9 What is the relationship between the *conductivity* of a material and its *resistivity*?
- 3.10 Determine the resistance of each of the following combinations.



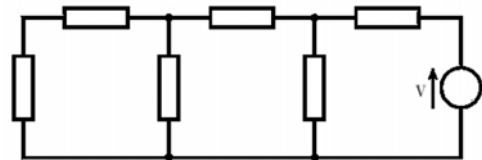
- 3.11 What resistance corresponds to $10\text{k}\Omega // 10\text{k}\Omega$?
- 3.12 Define the terms 'node', 'loop' and 'mesh'.
- 3.13 Label each of the nodes in the following arrangement with the letters A, B, C etc



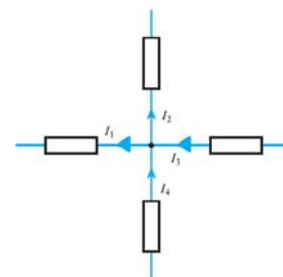
- 3.14 Having labelled each of the *nodes* in the previous exercise, use these labels to define each of the *loops* within the circuit and each of the *meshes*.
- 3.15 Given that $I_1 = 6 \text{ A}$, $I_3 = 8 \text{ A}$ and $I_4 = 5 \text{ A}$ determine the magnitude of I_2 in the following circuit.



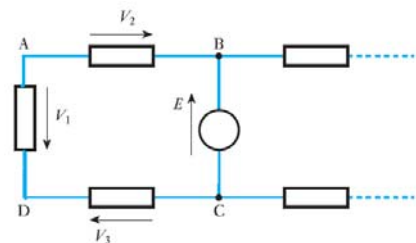
- 3.16 Given that $V_1 = 2 \text{ V}$, $V_3 = 4 \text{ V}$ and $E = 12 \text{ V}$, determine the magnitude of V_2 in the following circuit.



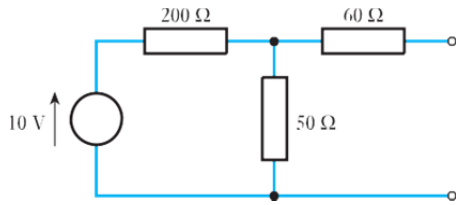
3.17 Derive Thévenin and Norton equivalent circuits for the following arrangements.



(a)

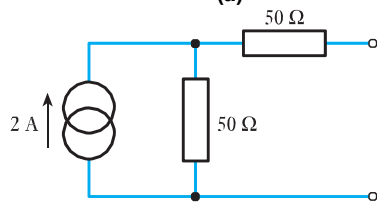

(b)

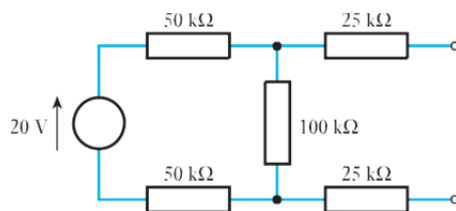

(c)


3.18 A two-terminal network is investigated by measuring the output voltage when connected to different loads. When a resistance of $12\ \Omega$ is connected across the output the output voltage is $16\ \text{V}$, and when a load of $48\ \Omega$ is connected the output voltage is $32\ \text{V}$. Use a graphical method to determine the Thévenin and Norton equivalent circuits of this arrangement.

3.19 Repeat Exercise 3.18 using a non-graphical approach.


3.20 The Thévenin equivalent circuit of an arrangement consists of a voltage source of $10\ \text{V}$ in series with a resistance of $100\ \Omega$. What would be an appropriate Norton equivalent circuit?

3.21 The Norton equivalent circuit of an arrangement consists of a current source of $25\ \text{mA}$ in parallel with a resistance of $2.5\ \text{k}\Omega$. What would be an appropriate Thévenin equivalent circuit?

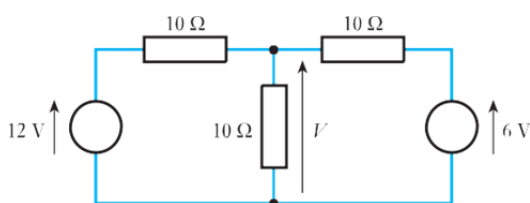
3.22 Use the principle of superposition to determine the voltage V in each of the following circuits.



(a)

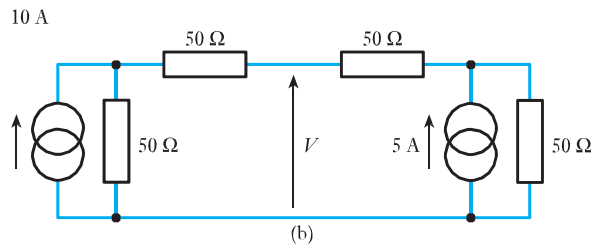


(b)

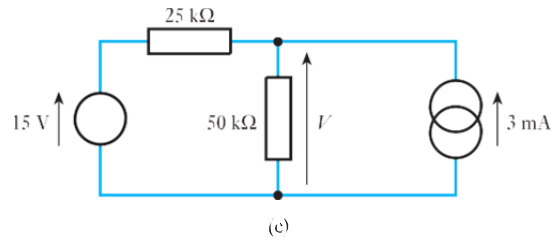


(c)

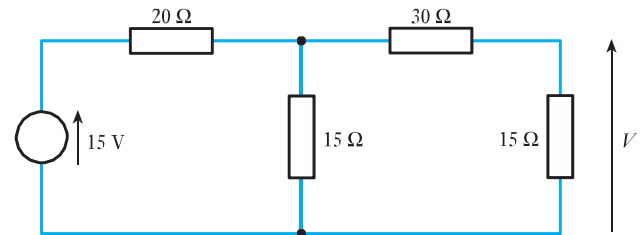
3.23 Use nodal analysis to determine the voltage V in the following circuit.



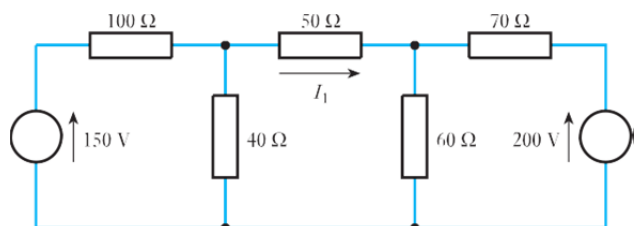
3.24 Use nodal analysis to determine the current I_1 in the following circuit.



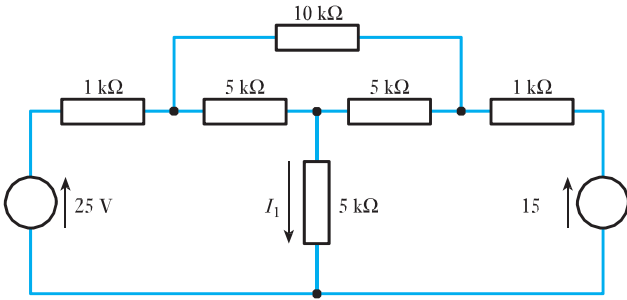
3.25 Use nodal analysis to determine the current I_1 in the following circuit



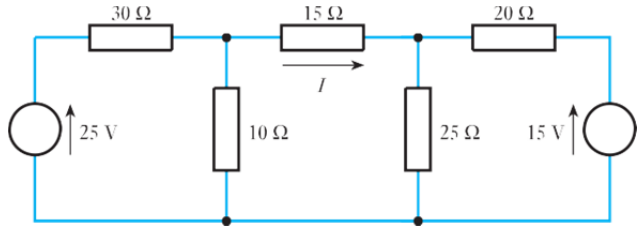
3.28 Use mesh analysis to determine the current I in the following circuit.



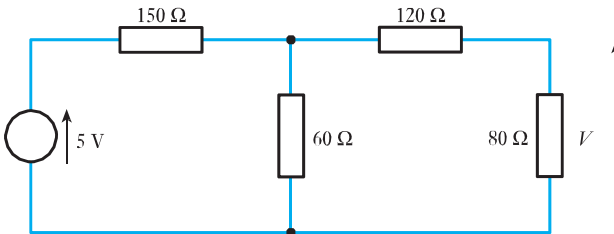3.26 Use mesh analysis to determine the voltage V in the following circuit.



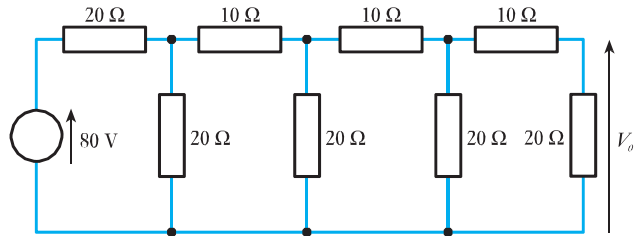3.29 Use an appropriate form of analysis to determine the voltage V_o in the following circuit.



3.27 Use mesh analysis to determine the voltage V in the following circuit.

