TUTORIAL 4 CAPACITANCE AND ELECTRIC FIELDS

- **4.1** Explain what is meant by a dielectric.
- **4.2** If electrons represent negative charge in a capacitor, what constitutes positive charge?
- **4.3** If the two plates of a capacitor are insulated from each other, why does it appear that under some circumstances a current flows between them?
- **4.4** Why does the presence of charge on the plates of a capacitor represent the storage of energy?
- **4.5** How is the voltage across a capacitor related to the stored charge?
- **4.6** What are the units of measurement of capacitance?
- 4.7 A 100 μF capacitor has 5 V across its terminals. What quantity of charge is stored in it?
- **4.8** A 22 μF capacitor holds 1 mC of stored charge. What voltage is seen across its terminals?
- **4.9** A capacitor has a voltage of 25 V across it when it holds 500 μ C of charge. What is its capacitance?

- **4.10** Why does a capacitor appear to pass AC signals while blocking DC signals?
- **4.11** How is the capacitance of a parallel-plate capacitor related to its dimensions?
- **4.12** The conducting plates of a capacitor are 5 X 15 mm and have a separation of 10 μm. What would be the capacitance of such a device if the space between the plates were filled with air?
- **4.13** What would be the capacitance of the device described in Exercise 4.12 if the space between the plates were filled with a dielectric with a relative permittivity of 200?
- **4.14** What is meant by stray capacitance, and why is this sometimes a problem?

4.15 Explain what is meant by an electric field and by electric field strength.

- **4.16** The plates of a capacitor have 250 V across them and have a separation of 15 μm. What is the electric field strength in the dielectric?
- **4.17** What is meant by dielectric strength?
- **4.18** Explain what is meant by electric flux and by electric flux density.
- **4.19** The plates of a capacitor are 15 x 35 mm and store a charge of 35 μC. Calculate the electric flux density in the dielectric.
- **4.20** Determine the effective capacitance of each of the following arrangements.











4.21

Given that $C_1 = 10 \ \mu\text{F}$, $C_2 = 20 \ \mu\text{F}$, $C_3 = 10 \ \mu\text{F}$ and $C_4 = 20 \ \mu\text{F}$, determine the voltages across the capacitors in the following arrangements.



- **4.22** Determine the charge stored in the capacitors C₁, C₂, C₃ and C₄ in the arrangements shown in exercise 4.21.
- **4.23** How is voltage related to current in a capacitor?
- **4.24** Explain what is meant by a time constant. Given that $R = 50 \text{ k}\Omega$ and $C = 10\mu\text{F}$, what is the time constant of the following arrangement?



- **4.25** If the resistor in the circuit of Exercise 4.24 was increased by a factor of 10 to 500 k Ω , what value of capacitor would be required to leave the time constant of the circuit unchanged?
- **4.26** Describe the relationship between the voltage across a capacitor and the current if the voltage is sinusoidal.
- **4.27** Give an expression for the energy stored in a charged capacitor.
- **4.28** A 5 mF capacitor is charged to 15 V. What is the energy stored in the capacitor?
- 4.29 A 50 μF capacitor contains 1.25 mC of charge. What energy is stored in the capacitor?