

CHAPTER 7 POWER IN AC CIRCUITS

Exercises

- 7.1** If a sinusoidal voltage with a frequency of 50 Hz is applied across a resistor, at what frequency does the instantaneous power supplied to the resistor vary?
- 7.2** A sinusoidal voltage $v = 10 \sin 377t$ is applied to a resistor of 50Ω . Calculate the average power dissipated in it.
- 7.3** If a sinusoidal voltage with a frequency of 50 Hz is applied across a capacitor, at what frequency does the instantaneous power supplied to the capacitor vary?
- 7.4** A sinusoidal voltage $v = 10 \sin 377t$ is applied across a capacitor of $1 \mu\text{F}$. Calculate the average power dissipated in it.
- 7.5** If a sinusoidal voltage with a frequency of 50 Hz is applied across an inductor, at what frequency does the instantaneous power supplied to the inductor vary?
- 7.6** A sinusoidal voltage $v = 10 \sin 377t$ is applied across an inductor of 1 mH . Calculate the average power dissipated in it.
- 7.7** Explain the meanings of the terms active power, apparent power and power factor.
- 7.8** The voltage across a component is 100 V r.m.s. and the current is 7 A r.m.s. If the current lags the voltage by 60° , calculate the apparent power, the power factor and the active power.
- 7.9** Explain the difference between the units of watts, VA and var.
- 7.10** A sinusoidal voltage of 100 V r.m.s. at 50 Hz is applied across a series combination of a 40Ω resistor and an inductor of 100 mH . Determine the r.m.s. current, the apparent power, the power factor, the active power and the reactive power.
- 7.11** A machine operates on a 250 V supply at 60 Hz ; it is rated at 500 VA and has a power factor of 0.8 . Determine the apparent power, the active power, the reactive power and the current in the machine.
- 7.12** Explain what is meant by power factor correction and explain why this is of importance in high-power systems.
- 7.13** Calculate the value of capacitor required to be added in parallel with the machine of Exercise 7.11 to achieve a power factor of 1.0 .
- 7.14** Calculate the value of capacitor required to be added in parallel with the machine of Exercise 7.11 to achieve a power factor of 0.9 .
- 7.15** A sinusoidal signal of 20 V peak at 50 Hz is applied to a load consisting of a 10Ω resistor and a 16 mH inductor connected in series. Calculate the power factor of this arrangement and the active power dissipated in the load.
- 7.16** Determine the value of capacitor needed to be added in series with the circuit of Exercise 7.11 to produce a power factor of 1.0 . Calculate the active power that would be dissipated in the circuit with the addition of such a capacitor.
- 7.17** Explain the difference between three- and four-conductor arrangements of three-phase power supplies.
- 7.18** Explain why it is not possible to calculate the power dissipated in an AC network by multiplying the readings of a voltmeter and an ammeter.
- 7.19** Explain how it is possible to measure power directly in a single-phase system.