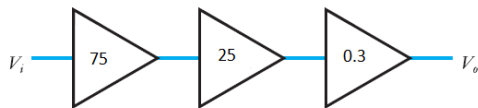


TUTORIAL 8 FREQUENCY CHARACTERISTICS OF AC CIRCUITS


- 8.1** What is meant by a 'two-port network', and what are the two ports?
- 8.2** Derive expressions for the voltage gain, current gain and power gain of a two-port network in terms of the input and output voltages, and the input and output currents.
- 8.3** Determine the voltage gain, current gain and power gain of the following arrangement.



- 8.4** Calculate the overall power gain of the following arrangement if the power gain of each stage is as shown in the diagram.




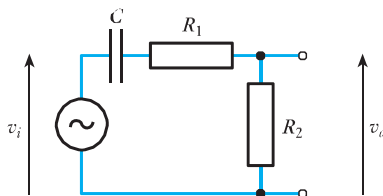- 8.5** For the arrangement shown in Exercise 8.4, determine the gain of each stage in decibels, and then compute the gain of the overall arrangement in decibels.
- 8.6** A circuit has a gain of 25 dB. What is its power gain (expressed as a simple ratio)?
- 8.7** A circuit has a gain of 25 dB. What is its voltage gain?
- 8.8** Calculate the reactance of a 1 μF capacitor at a frequency of 10 kHz, and the reactance of a 20 mH inductor at a frequency of 100 rad/s. In each case include the units in your answer.
- 8.9** Express an angular frequency of 250 rad/s as a cyclic frequency (in Hz).
- 8.10** Express a cyclic frequency of 250 Hz as an angular frequency (in rad/s).
- 8.11** Determine the transfer function of the following circuit.



8.12 A series RC circuit is formed from a resistor of $33\text{ k}\Omega$ and a capacitor of 15 nF . What is the time constant of this circuit?

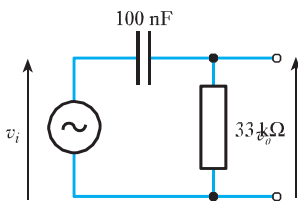
8.13 Calculate the time constant T , the angular cut-off frequency ω_c and the cyclic cut-off frequency f_c of the following arrangement. Is this a high- or a low-frequency cut-off?



8.14 Determine the frequencies that correspond to:


- an octave below 30 Hz ;
- two octaves above 25 kHz ;
- three octaves above 1 kHz ;
- a decade above 1 MHz ;
- two decades below 300 Hz ;
- three decades above 50 Hz .

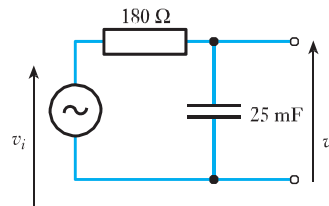8.15 Calculate the time constant T , the angular cut-off frequency ω_c and the cyclic cut-off frequency f_c of the following arrangement. Is this a high- or a low-frequency cut-off?




8.16 A parallel RL circuit is formed from a resistor of $150\ \Omega$ and an inductor of 30 mH . What is the time constant of this circuit?

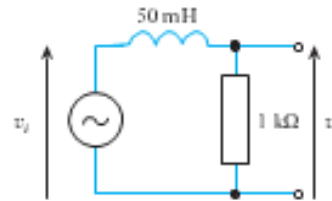8.17 Calculate the time constant T , the angular cut-off frequency ω_c and the cyclic cut-off frequency f_c of the following arrangement. Is this a high- or a low-frequency cut-off?



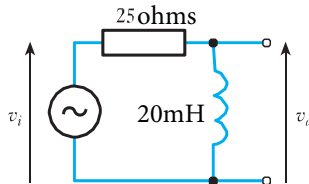- 8.18** Calculate the time constant T , the angular cut-off frequency ω_c and the cyclic cut-off frequency f_c of the following arrangement. Is this a high- or a low-frequency cut-off?




- 8.19** Sketch a straight-line approximation to the Bode diagram of the circuit of Exercise 8.18. Use this approximation to produce a more realistic plot of the gain and phase responses of the circuit.

- 8.20** A circuit contains three high-frequency cut-offs and two low-frequency cut-offs. What are the rates of change of gain of this circuit at very high and very low frequencies?

- 8.21** In the arrangement described in Exercise 8.20, what phase shift is produced at very high and very low frequencies?

- 8.22** Explain what is meant by the term 'resonance'.

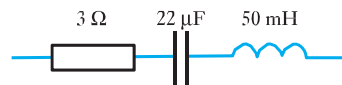- 8.23** Calculate the resonant frequency f_0 , the quality factor Q and the bandwidth B of the following circuit.



- 8.24** Calculate the resonant frequency f_0 , the quality factor Q and the bandwidth B of a parallel circuit with a resistor of 1 k Ω , an inductor of 50 mH and a capacitor of 22 μF .

- 8.25** Why is it more common to construct first order filters using combinations of resistors and capacitors, rather than resistors and inductors.

- 8.26** Explain the difference between a passive and an active filter.

- 8.27** Why are inductors often avoided in the construction of filters?

- 8.28** What form of active filter is optimised to produce a flat response within its pass band?

- 8.29** What form of active filter is optimised to produce a sharp transition from the pass band to the stop band?

- 8.30** What form of filter is optimised for a linear phase response?

- 8.31** Explain why stray capacitance and stray inductance affect the frequency response of electronic circuits.