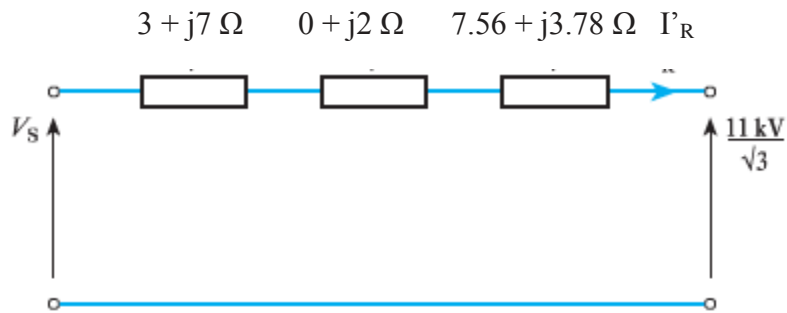


Example 1 - Solution

Since we are required to calculate the sending-end voltage, nominally 11 kV, we refer all impedances to the 11 kV side of the transformer:

$$0.01 \Omega \text{ becomes } 0.01 \times (11000/400)^2 = 7.56 \Omega$$

$$j0.005 \Omega \text{ becomes } j0.005 \times (11000/400)^2 = j 3.78 \Omega$$



Simplified diagram with impedances referred to 11kV

Hence,

$$Z_{\text{total}} = 10.56 + j 12.78$$

The next step is to calculate I_R (and I_S) from the three-phase power delivered,

250 kW:

$$\text{Power delivered} = 3V_R I_R \cos \Theta$$

$$250 \times 10^3 = 3 \times (400/\sqrt{3}) \times I_R$$

$$\mathbf{I_R = 360.8 \text{ A}}$$

However, in order to calculate the voltage drop down the equivalent network referred to 11 kV.

$$I'_R = 360.8 \times (400/11000) = 13.12 \text{ A}$$

$$\begin{aligned} V_S &= V_R + I_R Z_t \\ &= (11000/\sqrt{3}) + 13.12(10.56 + j12.78) \\ &= 6351 + 138.5 + j167.7 \\ &= 6489.5 + j167.7 \\ &= \mathbf{6491.7 \text{ V/ph}} \\ &\text{or } \mathbf{11.24 \text{ kV line}} \end{aligned}$$