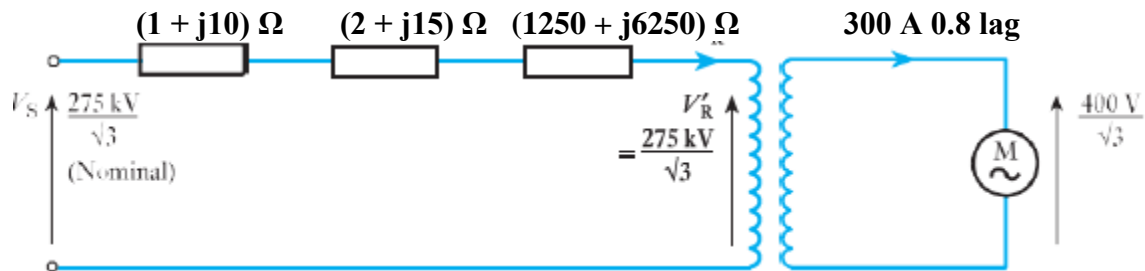


Example 2 - Solution

Since the sending-end voltage is to be calculated, we must refer the impedance of the 275/11 kV transformer to 275 kV:

$$Z' = (2 + j10) (275/11)^2 \Omega$$

$$Z' = 1250 + j6250 \Omega$$



The total impedance referred to 275 kV is now

$$Z_{\text{total}} = 1 + j10 + 2 + j15 + 1250 + j6250 \Omega$$

$$Z_{\text{total}} = 1253 + j6275 \Omega$$

The system volt drop per phase is now to be calculated. However, we first need to refer the current drawn by the motor to 275 kV

Actual motor current = 300 A at 400 V at 0.8 power factor

At 275 V,

$$I'_R = 300 (0.8 - j0.6) (400 / 275000) \text{ A}$$

$$I'_R = 0.35 - j 0.26 \text{ A}$$

$$V_S - V'_R + I'_R Z_T \text{ where } V'_R = 275 \text{ KV} / \sqrt{3}$$

$$V_S = 158.8 \times 10^3 + 2079 + j1872 \text{ V}$$

$$= 160.88 + j1.87 \text{ kV}$$

$$= \mathbf{160.9 \text{ V/ph}}$$

$$\text{or } \mathbf{278.6 \text{ kV line}}$$

In order to maintain a supply voltage of 400 V to the motor, the sending-end voltage has to be 278.6 kV.